
voltage divider


Malith Thiwanka

August 2020

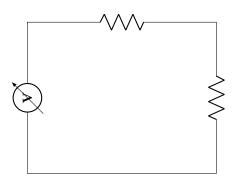

1 MANUALLY

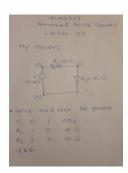Draw a circuit with elements and nodes. Write value of elements.



2 NG-SPICE

Simulate file with ng-spice.

* spice netlister for gnetlist V1 0 1 0.9 R2 1 2 10

R1 2 0 10 .END

